



CONESTOGA
Connect Life and Learning

DIGITAL DESIGN PRINCIPLES

LAB 6 – HALF ADDER & FULL ADDER

Name & Surname : Sinan KARACA

Date : 15 / 07 / 2021

Student ID : 8743013


INTRODUCTION

The purpose of the experiment is to implement half adder and full adder, each design consist of VHDL and verilog files. Each verilog or vhdl file consist of 1 bit adder components. The logic of the 1 adder components has been implement from truth table by applying K-Map method.

WORKING PRINCIPLE

HALF ADDER


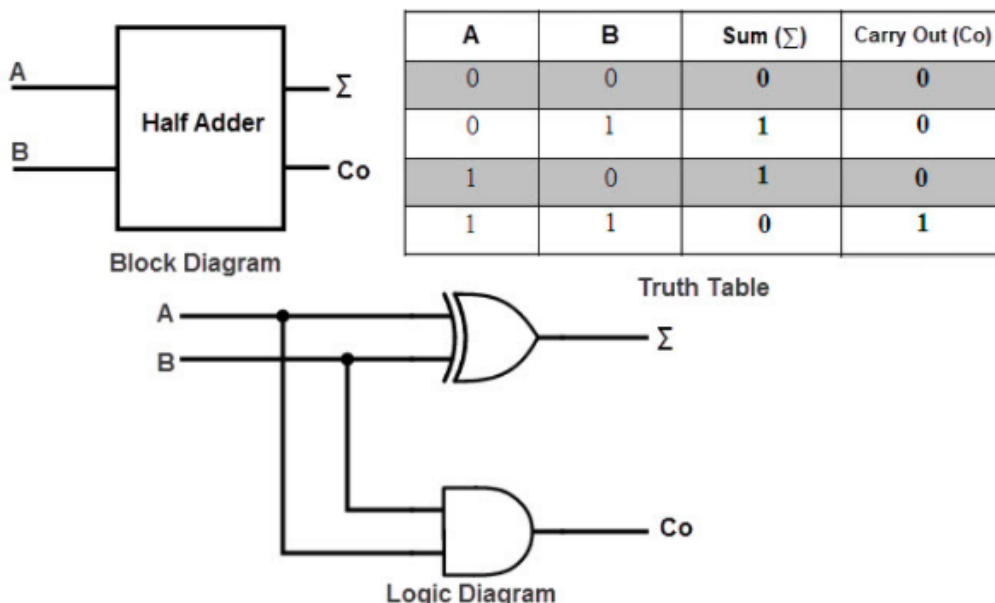
Each bit of half adder design are independent from each other, the logic of the design is shown down below,



The design consist of 4 oneBitComparator components, the logic circuit above has been designed with truth table of 4 bit magnitude comparator.

FULL ADDER

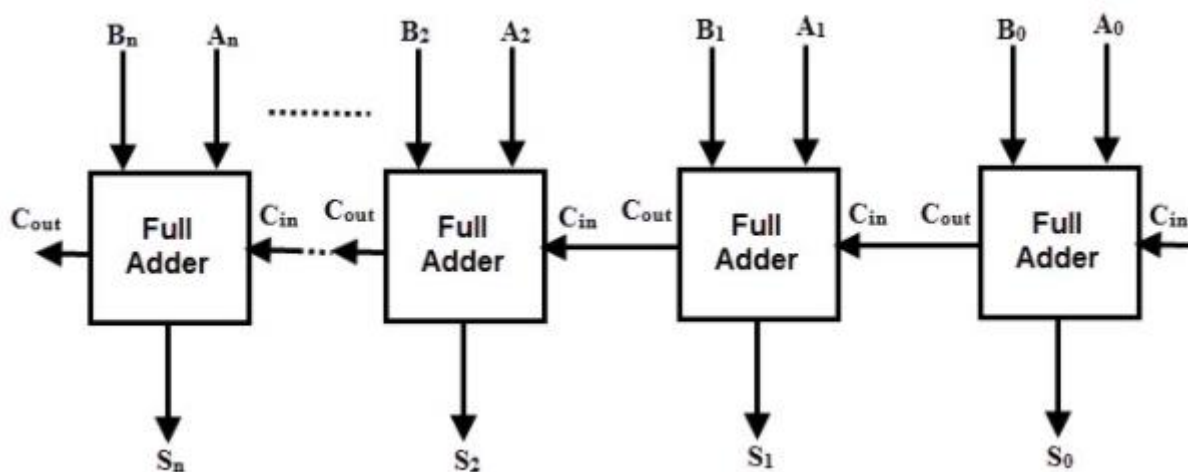 Each bit of full adder logic is shown down below, and also each bit of 4 bit full adder are dependent to each other. They are connected through Cout(0) to Cin(1).



VHDL CODE OF HALF ADDER

```
-----  
-- Project Name   : Half Adder  
-- File           : skaraca_lab4  
-- Creator        : Sinan KARACA  
-- Student number : 8743013  
-- Date           : 14.07.2021  
-----  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity halfAdder is  
    port(  
        InputA : in STD_LOGIC;  
        InputB : in STD_LOGIC;  
        Sum     : out STD_LOGIC;  
        Cout    : out STD_LOGIC);  
end halfAdder;  
  
architecture Behavioral of halfAdder is  
begin  
    Sum  <= InputA xor InputB;  
    Cout <= InputA and InputB;  
  
end Behavioral;
```

VHDL COMPONENT CODE OF HALF ADDER

```
-----  
-----  
-- Project Name   : 4 Bit Half Adder  
-- File           : skaraca_lab4  
-- Creator        : Sinan KARACA  
-- Student number : 8743013  
-- Date           : 14.07.2021  
-----  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity skaraca_Lab6 is  
    port(  
        sw      : in  STD_LOGIC_VECTOR(7 downto 0);  
        LED     : out STD_LOGIC_VECTOR(7 downto 0));  
end skaraca_Lab6;  
  
architecture Behavioral of skaraca_Lab6 is  
  
    --Component initialization  
    component halfAdder is  
        port(  
            InputA : in    STD_LOGIC;  
            InputB : in    STD_LOGIC;  
            Sum     : out   STD_LOGIC;  
            Cout    : out   STD_LOGIC);  
    end component halfAdder;  
  
    -- signals for outputs of halfadders  
    signal SumSignal  : STD_LOGIC_VECTOR(3 downto 0);  
    signal CoutSignal : STD_LOGIC_VECTOR(3 downto 0);  
  
begin  
  
    --Component declerations  
    -- LSB  
    H1: halfAdder port map (sw(4), sw(0), SumSignal(0), CoutSignal(0));  
    H2: halfAdder port map (sw(5), sw(1), SumSignal(1), CoutSignal(1));  
    H3: halfAdder port map (sw(6), sw(2), SumSignal(2), CoutSignal(2));  
    ---MSB  
    H4: halfAdder port map (sw(7), sw(3), SumSignal(3), CoutSignal(3));  
  
    -- 4 bit LED output  
    LED <= CoutSignal & SumSignal;  
  
end Behavioral;
```

VERILOG CODE OF HALF ADDER

```
////////////////////////////////////  
////////////////////////////////////  
// Project Name : HalfAdder  
// File : HalfAdder  
// Creator : Sinan KARACA  
// Student number: 8743013  
// Date : 14.07.2021  
////////////////////////////////////  
////////////////////////////////////  
  
module skaraca6_verilog(sw, LED);  
  
    input [7:0]sw;  
    output [7:0]LED;  
  
    wire [3:0]SumSignal;  
    wire [3:0]Cout;  
  
    HalfAdder(sw[4], sw[0] , SumSignal[0],Cout[0]);  
    HalfAdder(sw[5], sw[1] , SumSignal[1],Cout[1]);  
    HalfAdder(sw[6], sw[2] , SumSignal[2],Cout[2]);  
    HalfAdder(sw[7], sw[3] , SumSignal[3],Cout[3]);  
  
    assign LED = {Cout, SumSignal};  
  
endmodule
```

VERILOG COMPONENT CODE OF HALF ADDER

```
////////////////////////////////////  
////////////////////////////////////  
// Project Name : HalfAdder  
// File : HalfAdder  
// Creator : Sinan KARACA  
// Student number: 8743013  
// Date : 17.06.2021  
////////////////////////////////////  
////////////////////////////////////  
  
module HalfAdder(InputA, InputB, Sum, Cout);  
  
    input InputA, InputB;  
    output Sum;  
    output Cout;  
  
    assign Sum = InputA ^ InputB;  
    assign Cout = InputA & InputB;  
  
endmodule
```

VHDL CODE OF FULL ADDER

```
-- File           : skaraca_lab4
-- Creator        : Sinan KARACA
-- Student number : 8743013
-- Date          : 14.07.2021
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity skaraca_Lab6 is
    port(
        sw      : in  STD_LOGIC_VECTOR(7 downto 0);
        LED     : out STD_LOGIC_VECTOR(4 downto 0));
end skaraca_Lab6;

|
architecture Behavioral of skaraca_Lab6 is

--Component initialization
component fullAdder is
    port(
        InputA : in  STD_LOGIC;
        InputB : in  STD_LOGIC;
        Cin    : in  STD_LOGIC;
        Sum     : out STD_LOGIC;
        Cout    : out STD_LOGIC);
end component fullAdder;

-- Signals for outputs of halfadders
signal SumSignal : STD_LOGIC_VECTOR(3 downto 0);
signal CoutSignal : STD_LOGIC_VECTOR(3 downto 0);

begin

--Component declarations
H1: fullAdder port map (sw(4), sw(0), '0', SumSignal(0), CoutSignal(0));
H2: fullAdder port map (sw(5), sw(1), CoutSignal(0), SumSignal(1), CoutSignal(1));
H3: fullAdder port map (sw(6), sw(2), CoutSignal(1), SumSignal(2), CoutSignal(2));
H4: fullAdder port map (sw(7), sw(3), CoutSignal(2), SumSignal(3), CoutSignal(3));

-- 4 bit LED output
LED <= CoutSignal(3) & SumSignal ;
```

VHDL COMPONENT CODE OF FULL ADDER

```
-----  
-- Project Name   : Full Adder  
-- File           : skaraca_lab4  
-- Creator        : Sinan KARACA  
-- Student number : 8743013  
-- Date           : 14.07.2021  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity fullAdder is  
    port(  
        InputA : in STD_LOGIC;  
        InputB : in STD_LOGIC;  
        Cin     : in STD_LOGIC;  
        Sum     : out STD_LOGIC;  
        Cout    : out STD_LOGIC);  
end fullAdder;  
  
architecture Behavioral of fullAdder is  
begin  
    Sum  <= InputA xor InputB xor Cin;  
    Cout <= (InputA and InputB) or (InputA and Cin) or (InputB and Cin) ;  
  
end Behavioral;
```

VERILOG CODE OF FULL ADDER

```
////////////////////////////////////  
////////////////////////////////////  
// Project Name   : Full Adder  
// File           : Full Adder  
// Creator        : Sinan KARACA  
// Student number : 8743013  
// Date           : 14.07.2021  
////////////////////////////////////  
////////////////////////////////////  
  
module skaraca6_verilog(sw, LED);  
  
    input [7:0]sw;  
    output [4:0]LED;  
  
    wire [3:0]sumSignal;  
    wire [3:0]Cout;  
  
    fullAdder(sw[4], sw[0] , 1'b0 , SumSignal[0],Cout[0]);  
    fullAdder(sw[5], sw[1] , Cout[0], SumSignal[1],Cout[1]);  
    fullAdder(sw[6], sw[2] , Cout[1], SumSignal[2],Cout[2]);  
    fullAdder(sw[7], sw[3] , Cout[2], SumSignal[3],Cout[3]);  
  
    assign LED = {Cout[3], sumSignal};  
  
endmodule
```


VERILOG COMPONENT CODE OF FULL ADDER

```
// Project Name : fullAdder
// File : fullAdder
// Creator : Sinan KARACA
// Student number: 8743013
// Date : 17.06.2021


module fullAdder(InputA, InputB, Cin, Sum, Cout);

    input InputA, InputB , Cin;
    output Sum;
    output Cout;


    assign Sum = InputA ^ InputB ^ Cin;
    assign Cout = (InputA & InputB) | (InputA & cin) | (InputB & cin) ;

endmodule
```

PIN ASSIGNMENT

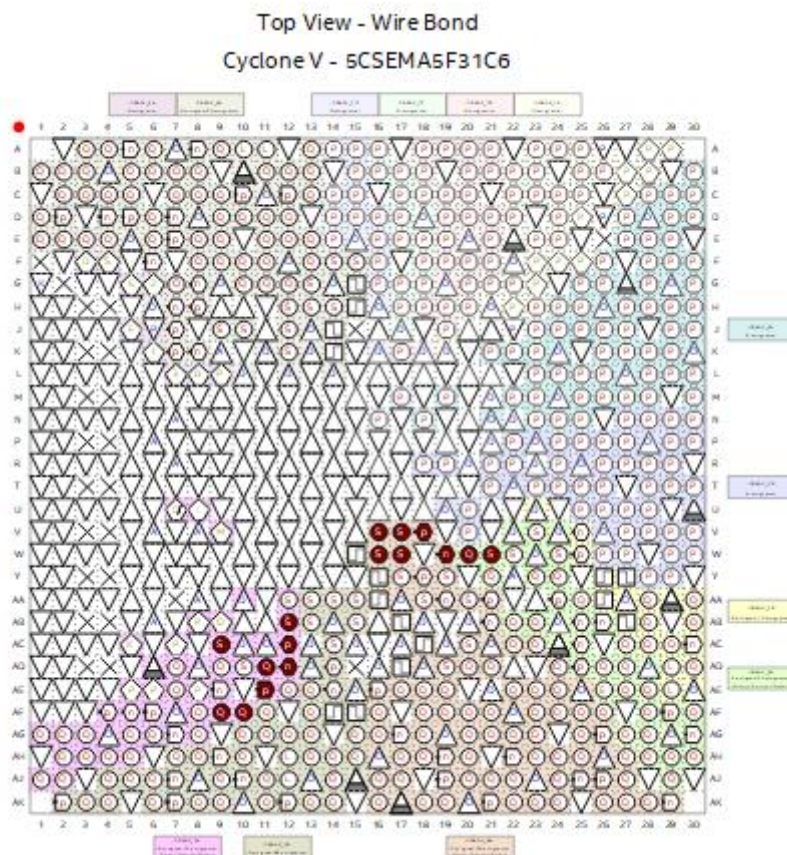

Full Adder

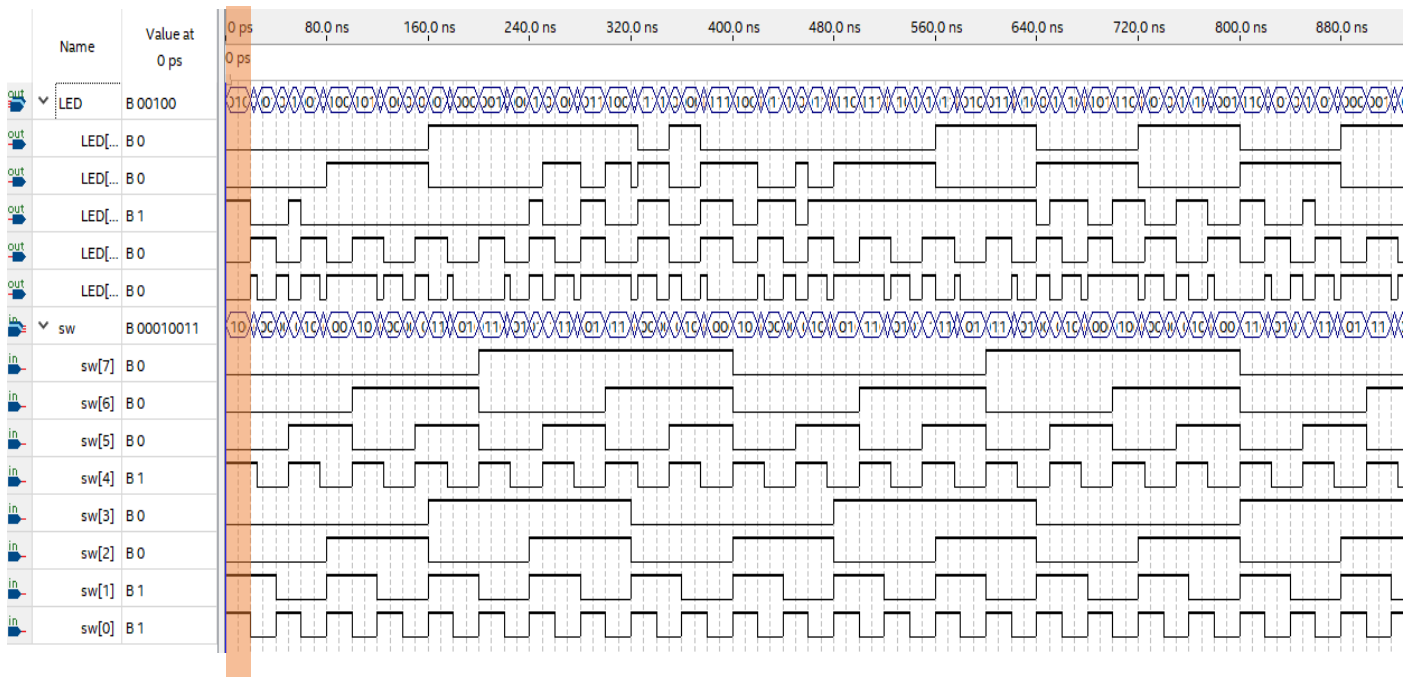

Last digits of my student id is “1” , “3” , it is shown above. The result of full adder is Sum = 0100 and Cout = 0.

CONCLUSION

Design of full adder and half adder has been experienced in the this experiment, 4 different codes has been written and run, each has its own components. Components consist of logical operations, as they are implemented from K-Map method.