



**CONESTOGA**  
Connect Life and Learning

## **DIGITAL DESIGN PRINCIPLES**

### **LAB 8 – SHIFT REGISTER**

---

**Name & Surname :** Sinan KARACA

**Date :** 29 / 07 / 2021

**Student ID :** 8743013

---

### **INTRODUCTION**

The purpose of the experiment is to design right and left shift register, the design has been done with functions of VHDL and Verilog.

### **WORKING PRINCIPLE**

The design is implemented with the functions of VHDL and Verilog, there are 3 different mode of working principle. When selection is “00” it means NULL, “01” it means 1 bit left shift, “10” it means 1 bit right shift and “11” it means load the 4 bits to output.

Switch case has been implemented for selection left or right, it is working under the clock process. Clock process is being triggered with the positive rising edge of KEY clock.

# VHDL MAIN PROGRAM

```
-----  
-----  
-- Project Name   : Shift Register  
-- File           : skaraca_lab8  
-- Creator        : Sinan KARACA  
-- Student number : 8743013  
-- Date           : 29.07.2021  
-----  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity skaraca_Lab8 is  
    port(  
        SW      : in STD_LOGIC_VECTOR (7 downto 0);  
        Clock    : in STD_LOGIC;  
        LEDR     : out STD_LOGIC_VECTOR(3 downto 0));  
end skaraca_Lab8;  
  
architecture Behavioral of skaraca_Lab8 is  
  
    function shiftLeft(  
        threeBitLeft:in STD_LOGIC_VECTOR(2 downto 0);  
        registerBitLeft:in STD_LOGIC)  
        return STD_LOGIC_VECTOR is variable output: STD_LOGIC_VECTOR(3 downto 0);  
    begin  
        output := threeBitLeft & registerBitLeft;  
        return output;  
    end shiftLeft;  
  
    function shiftRight(  
        threeBitRight:in STD_LOGIC_VECTOR(2 downto 0);  
        registerBitRight:in STD_LOGIC)  
        return STD_LOGIC_VECTOR is variable output: STD_LOGIC_VECTOR(3 downto 0);  
    begin  
        output := registerBitRight & threeBitRight ;  
        return output;  
    end shiftRight;
```

```

function Load(
    fourBit:in STD_LOGIC_VECTOR(3 downto 0))
return STD_LOGIC_VECTOR is variable output: STD_LOGIC_VECTOR(3 downto 0);
begin
    output := fourBit;
    return output;
end Load;

signal R : STD_LOGIC_VECTOR(3 downto 0);
signal S : STD_LOGIC_VECTOR(1 downto 0);

begin
    process(Clock, S, Sw)
    begin
        S <= Sw(7 downto 6);
        LEDR <= R;

        if rising_edge(Clock) then
            case S is
                when "00" =>
                    NULL;
                when "01" =>
                    R <= shiftLeft(R(2 downto 0), Sw(0));

                when "10" =>
                    R <= shiftRight(R(3 downto 1), Sw(5));

                when "11" =>
                    R <= Load (Sw(4 downto 1));

                when others =>
                    NULL;
            end case;
        end if;
    end process;

end Behavioral;

```

# VERILOG MAIN PROGRAM

```
////////////////////////////////////
////////////////////////////////////
// Project Name   : Shift Register
// File          : skaraca_lab8
// Creator       : Sinan KARACA
// Student number: 8743013
// Date         : 29.07.2021
////////////////////////////////////
////////////////////////////////////

module skaraca_Lab8(SW,Clock,LEDR);

    input [7:0]SW;
    input Clock;
    output [3:0]LEDR;

    wire [3:0]R;
    wire [1:0]S;

    function [3:0] shiftLeft;
        input [2:0]threeBitLeft ;
        input registerBitLeft;

        begin

            shiftLeft[3:0] = { threeBitLeft[2:0], registerBitLeft};

        end
    endfunction

    function [3:0] shiftRight;
        input [2:0] threeBitRight;
        input registerBitRight;

        begin

            shiftRight[3:0] = { registerBitRight, threeBitRight[2:0] };

        end
    endfunction

    function [3:0] Load;
        input [3:0] threeBitRight;

        begin

            Load = threeBitRight;

        end
    endfunction

    // Asynchronous Assignments
    assign S = SW[7:6];
    assign LEDR = R;


    //Clock Assignments
    always @ (posedge Clock) begin
        case(S)

            2'b01      : R = shiftLeft(R[2:0], SW[0]);
            2'b10      : R = shiftRight(R[3:1], SW[5]);
            2'b11      : R = Load(SW[4:1]);

        endcase
    end


endmodule
```

 Top View - Wire Bond  
Cyclone V - 5CSEMA5F31C6



in	Clock	Input	PIN_AA14	3B	B3B_NO	PIN_AA14	2.5 V		12mA (default)	
out	LEDR[3]	Output	PIN_W17	4A	B4A_NO	PIN_W17	2.5 V		12mA (default)	1 (default)
out	LEDR[2]	Output	PIN_W19	4A	B4A_NO	PIN_W19	2.5 V		12mA (default)	1 (default)
out	LEDR[1]	Output	PIN_W20	5A	B5A_NO	PIN_W20	2.5 V		12mA (default)	1 (default)
out	LEDR[0]	Output	PIN_W21	5A	B5A_NO	PIN_W21	2.5 V		12mA (default)	1 (default)
in	SW[7]	Input	PIN_AB12	3A	B3A_NO	PIN_AB12	2.5 V		12mA (default)	
in	SW[6]	Input	PIN_AC12	3A	B3A_NO	PIN_AC12	2.5 V		12mA (default)	
in	SW[5]	Input	PIN_AF9	3A	B3A_NO	PIN_AF9	2.5 V		12mA (default)	
in	SW[4]	Input	PIN_AF10	3A	B3A_NO	PIN_AF10	2.5 V		12mA (default)	
in	SW[3]	Input	PIN_AD11	3A	B3A_NO	PIN_AD11	2.5 V		12mA (default)	
in	SW[2]	Input	PIN_AD12	3A	B3A_NO	PIN_AD12	2.5 V		12mA (default)	
in	SW[1]	Input	PIN_AE11	3A	B3A_NO	PIN_AE11	2.5 V		12mA (default)	
in	SW[0]	Input	PIN_AC9	3A	B3A_NO	PIN_AC9	2.5 V		12mA (default)	

## SIMULATION WAVEFORM

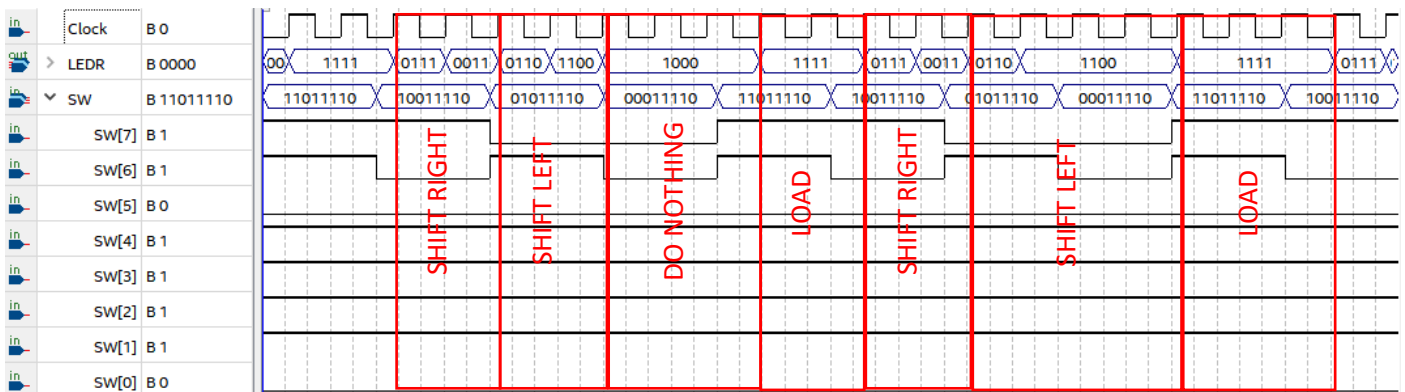

Simulation waveform shows the all combinations of 4 different scenarios.

SW[1-4] = "1111" , so we are suppose to see "1111" when it is loaded.

And also SW[0] and SW[5] is equal to "0", so we are suppose to see zeros when it is shifted.

## CONCLUSION

Design of the shift register has been doen in this experiment. Each operation has been done with functions. The function is not necessary to use, I used the functions for learning deeply about VHDL and Verilog.